

# A Simple Implementation

*CPE380, Fall 2025*

**Hank Dietz**

<http://aggregate.org/hankd/>

# Where Is This Stuff?

- Not in the text per se...
- Primary reference is:

<http://aggregate.org/CPE380/refs3S25.html>

- Textbook appendix B reviews CPE282 stuff...

# A Dumb Implementation

- A design like I learned as an undergrad...
  - Can be built with a pile of TTL parts
  - Can execute MIPS instructions
  - Slow; many clock cycles per instruction
- The key parts:
  - Memory
  - Processor
  - I/O – which we'll ignore for now...


# Our Favorite Gates

- In CPE282, you never used one of these:






but they help keep signals digital...

- In CPE380, we use lots of these:

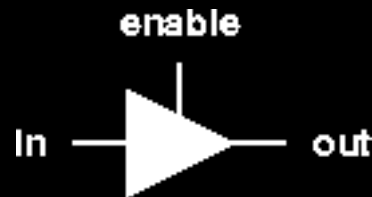

to make **bus** and **mux** structures...

# Tri-State (& Open Collector)

 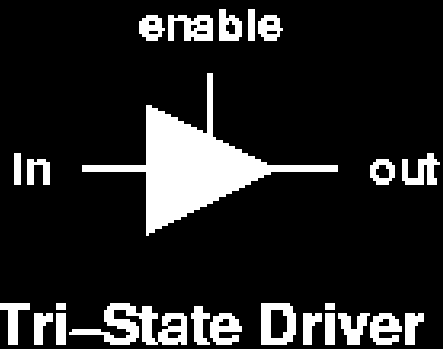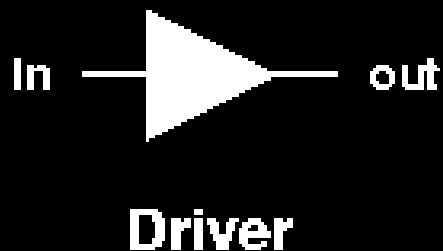


| In | enable | A   | B   | out    |
|----|--------|-----|-----|--------|
| X  | 0      | off | off | Z      |
| 0  | 1      | off | on  | 0      |
| 1  | 1      | on  | off | 1      |
|    |        | on  | on  | short! |


Open Collector replaces A with a resistor

TTL Input floats high; CMOS doesn't

# Processor/Memory Interface

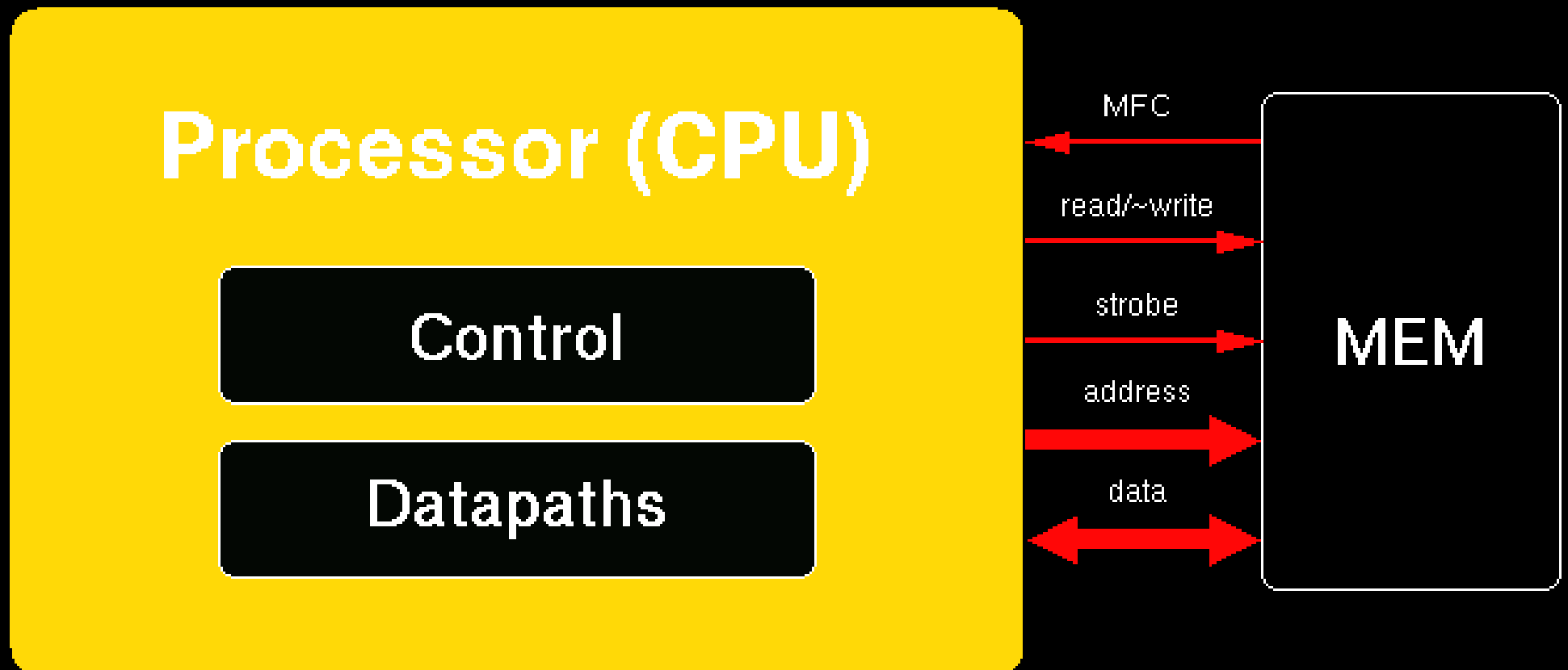

# A bit Of SRAM (D Flip Flop)

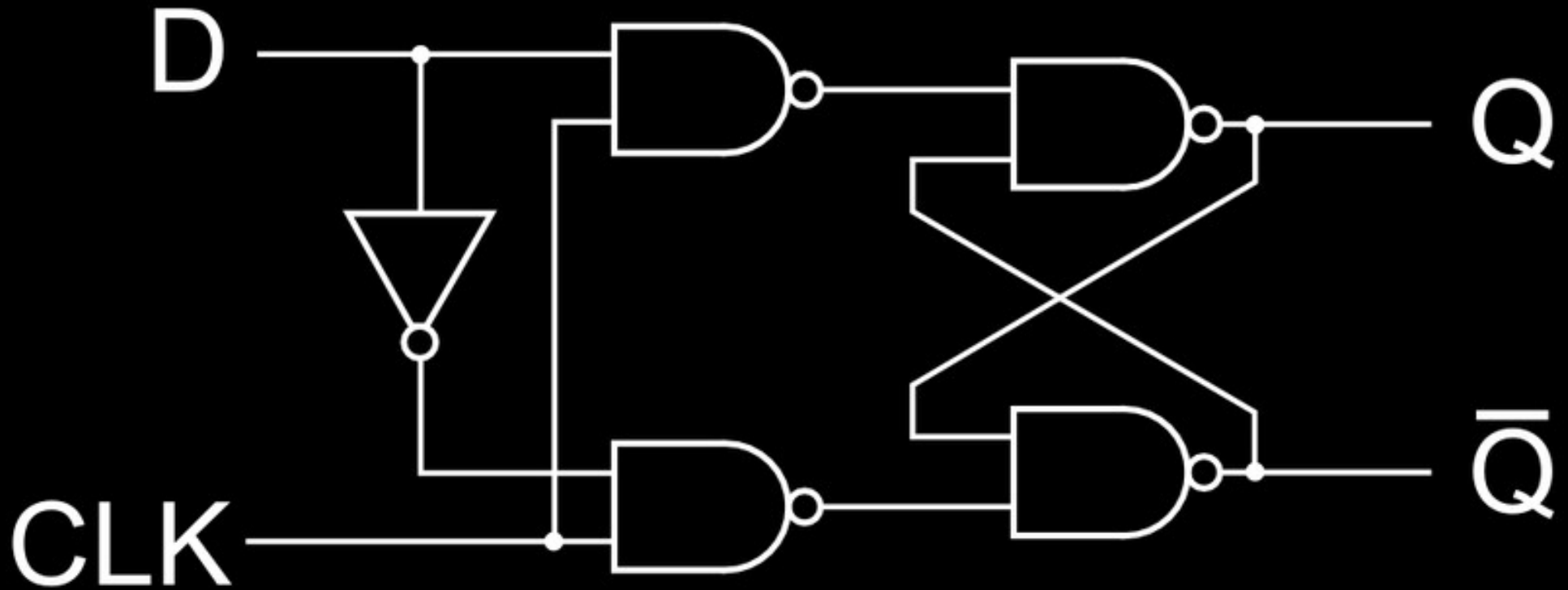


# In Verilog


```
module DFF(q, d, clk);  
input d, clk;  
output reg q;  
  
always @(posedge clk) q <= d;  
endmodule
```



# A Simple Memory

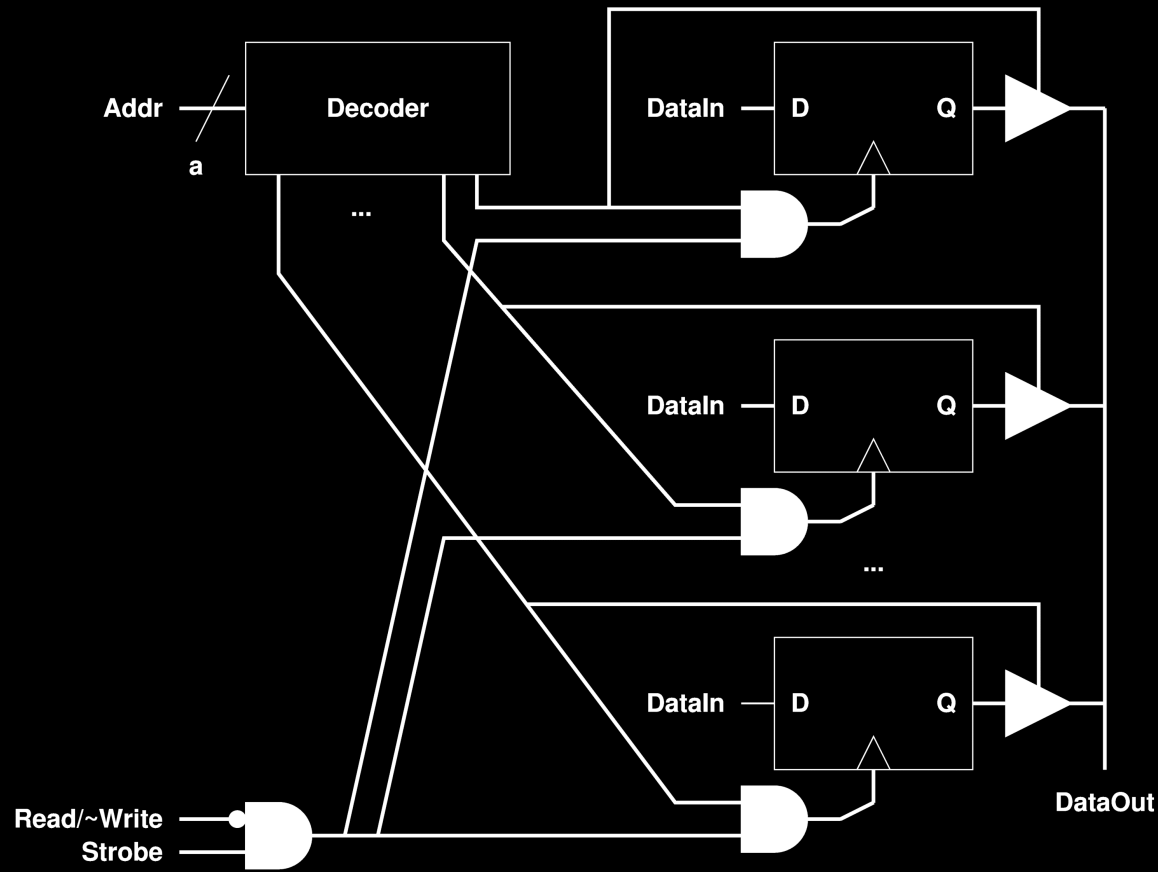

# What If Data Is Bidirectional?

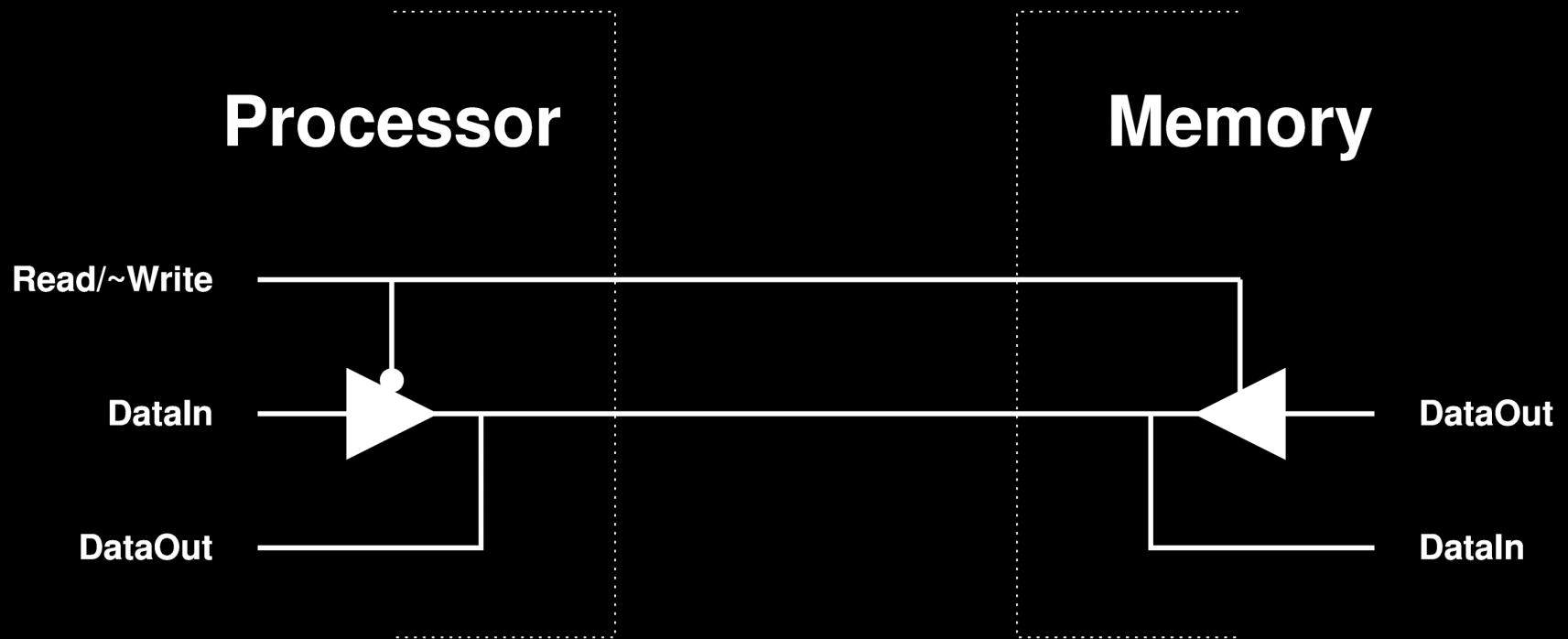

# In Verilog

```
module memory(mfc, dread, dwrite, addr, rnotw, strobe);
output reg mfc; output reg [7:0] dread;
input [7:0] dwrite; input [15:0] addr;
input rnotw, strobe;
reg [7:0] m [65535:0];


always @(posedge strobe) begin
    mfc = 0;
    if (rnotw) begin
        dread <= m[addr];
        mfc = #4 1; // delay 4 units of simulated time
    end else begin
        m[addr] <= dwrite;
    end
end
endmodule
```

# Parametric Verilog

```
module memory(mfc, dread, dwrite, addr, rnotw, strobe);
parameter ABITS = 8; parameter DBITS = 16;
output reg mfc; output reg [DBITS-1:0] dread;
input [DBITS-1:0] dwrite; input [ABITS-1:0] addr;
input rnotw, strobe;
reg [DBITS-1:0] m [(1<<ABITS)-1:0];


always @(posedge strobe) begin
    mfc = 0;
    if (rnotw) begin
        dread <= m[addr];
        mfc = #4 1; // delay 4 units of simulated time
    end else begin
        m[addr] <= dwrite;
    end
end
endmodule
```

# A bit Of DRAM

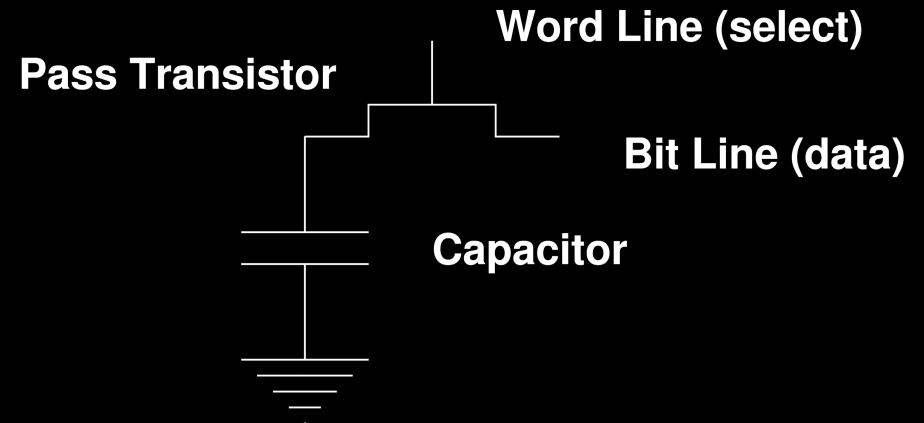

- Data to Vcc to store 1
- Data to Gnd to store 0
- Read: dump charge, amplify, & threshold
  - Analog – slow & noise sensitive
  - Destructive (need to refresh value)
- Charge slowly leaks (need to refresh)

# Inside The Processor

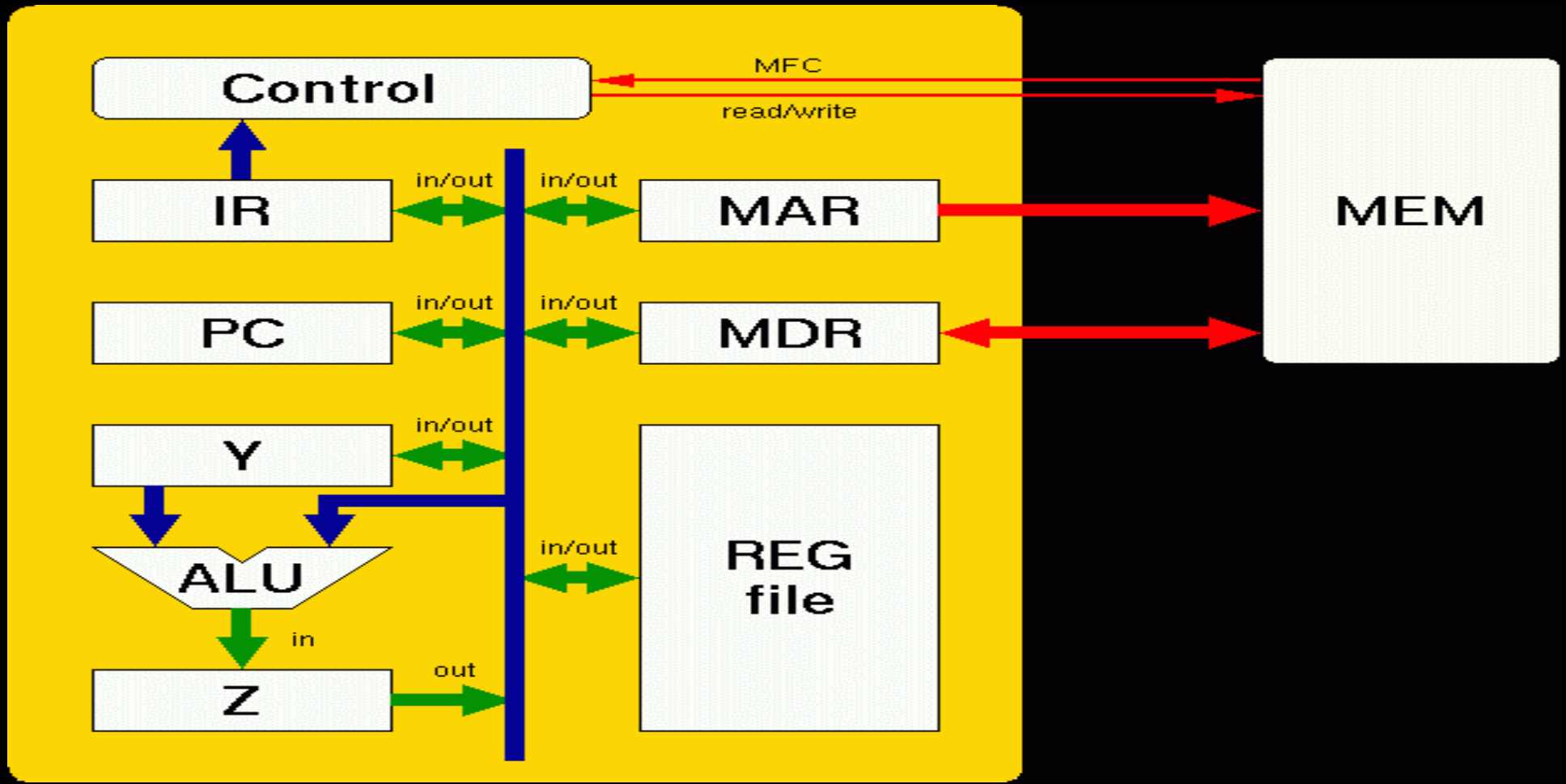

# In Verilog

```
`define WORD      [31:0]    // size of a data word
`define STATENO   [31:0]    // size of a state number

module module processor(halt, reset, clk);
output reg halt;
input reset, clk;
reg `WORD IR, PC, MAR, MDR, Y, ALUMUX, ALUZ;
reg rnotw, strobe;
wire mfc;
wire `WORD dread;
reg `WORD addr;
reg `STATENO STATE;
...
memory mainmem(mfc, dread, MDR, MAR, rnotw, strobe);
...
endmodule
```

# Something To Run It...

```
module testbench;
reg reset = 1;
reg clk = 0;
wire halt;

processor PE(halt, reset, clk);

initial begin
    #1 reset = 0;
    while (!halt) begin
        #1 clk = 1;
        #1 clk = 0;
    end
end
endmodule
```



| REGISTER control signal | Effect   |
|-------------------------|--|
| ALUadd                  | Configures the ALU to add its inputs   |
| ALUand                  | Configures the ALU to bitwise AND its inputs   |
| ALUxor                  | Configures the ALU to bitwise eXclusive OR its inputs  |
| ALUor                   | Configures the ALU to bitwise OR its inputs  |
| ALUsl                   | Configures the ALU to shift left logical; the result is (bus << Y)   |
| ALUslt                  | Configures the ALU to compare its inputs; the result is (Y < bus)  |
| ALU srl                 | Configures the ALU to shift right logical; the result is (bus >> Y)  |
| ALUsub                  | Configures the ALU to subtract the bus input from Y  |
| CONST( <i>value</i> )   | Places the constant <i>value</i> onto the bus  |
| HALT                    | Halt the machine (stop the simulator without error) at the end of the current state  |
| IRaddout                | Tri-state enables the portion of the Instruction Register that contains the (26 bit, MIPS "J" format) address, along with the top 6 bits of the Program Counter, to be driven onto the bus   |
| IRimmedout              | Tri-state enables the portion of the Instruction Register that contains the (16 bit, MIPS "I" format) 2's complement immediate value to be sign-extended to 32 bits and driven onto the bus  |
| IRin                    | Latches the bus data into the Instruction Register at the trailing edge of the clock cycle   |
| IRoffsetout             | Tri-state enables the Instruction Register's shifted and sign extended value from the offset field to be driven onto the bus (used for branches)   |
| JUMP( <i>label</i> )    | Microcode jump to <i>label</i>   |
| JUMPop                  | Microcode jump to label named like the opcode; e.g., if an "Addi" is in the IR, jumps to the microcode label Addi  |
| MARin                   | Latches the bus data into the Memory Address Register at the trailing edge of the clock cycle  |
| MARout                  | Tri-state enables the Memory Address Register's output to be driven onto the bus   |
| MDRin                   | Latches the bus data into the Memory Data Register at the trailing edge of the clock cycle   |
| MDRout                  | Tri-state enables the Memory Data Register's output to be driven onto the bus  |
| MEMread                 | Initiate a memory read from the address in the MAR; here, you may assume that the memory will take 2 clock cycles to respond   |
| MEMwrite                | Initiate a memory write using the data in the MDR and the address in the MAR; in this simple design, you may assume that a memory write takes precisely 1 clock cycle  |
| PCin                    | Latches the bus data into the Program Counter at the trailing edge of the clock cycle  |
| PCinif0                 | Only if the value in Z is zero, latch the bus data into the Program Counter at the trailing edge of the clock cycle  |
| PCout                   | Tri-state enables the Program Counter's output to be driven onto the bus   |
| REGin                   | Latches the bus data into whichever register is selected by SELrs, SELrt, or SELrd; the value is latched at the trailing edge of the clock cycle   |
| REGout                  | Tri-state enables the output of whichever register is selected by SELrs, SELrt, or SELrd; the selected value is driven onto the bus  |
| SELrs                   | Selects the rs field of the IR to be used to control the register file's decoder   |
| SELrt                   | Selects the rt field of the IR to be used to control the register file's decoder   |
| SELrd                   | Selects the rd field of the IR to be used to control the register file's decoder   |
| UNTILmfc                | Repeat this state until the memory has issued a memory fetch complete signal, indicating that the fetched value will be valid to read from the MDR in the next clock cycle   |
| Yin                     | Latches the bus data into the Y register at the trailing edge of the clock cycle; this register is needed because, with only one bus, one of the two operands for a binary operation (e.g., Add) must come from somewhere other than the bus |
| Yout                    | Tri-state enables the Y register's output to be driven onto the bus  |
| Zin                     | The ALU is always producing a result, but we only make note of that result if we latch the ALU's output into the Z register at the trailing edge of the clock cycle  |
| Zout                    | Tri-state enables the Z Register's output to be driven onto the bus  |

# Control Logic

- A big state machine (spec. by names)
  - Begins by fetching instruction
  - Decoding instruction sends us to particular instruction's state sequence
  - Ends by going to fetch next instruction
- Instruction decode logic
  - when** *mask match lab*
  - Applied in state with **JUMPNOP**
  - if  $((IR \ \& \ mask) == match)$  goto *lab*;

# Instruction Fetch Sequence

- Not dependent on instruction – can't be
- Also does  $PC+=4$

```
Start: PCout, MARin, MEMread, Yin  
CONST(4), ALUadd, Zin, UNTILmfc  
MDRout, Irin  
JUMPNOP, Zout, Pcin  
HALT /* illegal inst. */
```

# MIPS Register Add

- `add $rd,$rs,$rt`
- Means  $rd=rs+rt$

Add: SELrs,REGout,Yin  
SELrt,REGout,ALUadd,Zin  
Zout,SELrd,REGin,JUMP(Start)

# MIPS Register And

- `and $rd,$rs,$rt`
- Means  $rd = rs \& rt$

And: SELrs,REGout,Yin  
SELrt,REGout,ALUand,Zin  
Zout,SELrd,REGin,JUMP(Start)

# MIPS Load Word

- $lw\ \$rt, immed(\$rs)$
- Means  $rt = mem[immed + rs]$

Lw: SELrs, REGout, Yin  
IRIMMEDout, ALUadd, Zin  
Zout, MARin, MEMread  
UNTILmfc  
MDRout, SELrt, REGin, JUMP(Start)

# MIPS Store Word

- $sw\ \$rt, immed(\$rs)$
- Means  $mem[immed+rs]=rt$
- Don't have to wait for write to complete

Sw: SELrt, REGout, MDRin  
SELrs, REGout, Yin  
IRIMMEDout, ALUadd, Zin  
Zout, MARin, MEMwrite, JUMP(Start)

# Timing

- Clock period determined by slowest path in any state – try to minimize variation
- Number of clock cycles/instruction (CPI) is determined by counting
  - Not just count of states passed through
  - Time passed waiting counts (UNTILmfc)
- Clock period and CPI usually trade off; higher Hz often achieved by higher CPI



# Clock Period

- Assume the critical state is:

SELrt , REGout , MDRin , ALUadd , Zin

- The paths are:

SELrt > REGout > MDRin

SELrt > REGout > ALUadd > Zin

# Reducing Clock Period

- Increase clock speed by replacing:

SELrt, REGout, MDRin, ALUadd, Zin

- With:

SELrt, REGout, MDRin  
MDRout, ALUadd, Zin

# Counting CPI

- Instruction fetch time counts
- Time between MEMread and UNTILmfc

Lw: SELrs,REGout,Yin +1  
IRIMMEDout,ALUadd,Zin +1  
Zout,MARin,MEMread +1  
UNTILmfc +?  
MDRout,SELrt,REGin,JUMP(Start) +1

# Cycle-Accurate Simulation

- Custom-built full simulator for CPE380
  - Textual state machine specification
  - Can define signal delays
  - Can define initial & final conditions
  - Built-in mini MIPS assembler

<http://aggregate.org/CPE380/refss.html>

- Actual simulator is live at

<http://garage.ece.engr.uky.edu:10043/cgi-bin/simple.cgi>

# A Verilog Implementation

- Design for simulation, not rendering HW
- Key ideas:
  - ``define` control signals & constants
  - `module memory(...);`  
Models main memory
  - `module processor(halt, reset, clk);`  
Models the complete processor
  - `module bench;`  
Drives the simulation

# Verilog Simulation

- Don't have to go low level:

<http://aggregate.org/CPE380/multiS25.html>

- Don't have to feed it raw bits either;  
here's a (slightly mutant) MIPS assembler:

<http://aggregate.org/CPE380/mipsaik.html>

but I don't expect you to be using AIK