

# An Introduction To Verilog

*CPE480/EE480/CS480G, Fall 2019*

**Hank Dietz**

<http://aggregate.org/hankd/>

# References

- IEEE 1364-2005
- **Verilog HDL** by Samir Palnitkar, ISBN-978-0132599702
- Various Verilog materials online, e.g.:  
<http://www.asic-world.com/verilog/>
- The Icarus Verilog wiki
- The course WWW site:

<http://aggregate.org/EE480/>


# A Little History

- Philip Moorby created Verilog around 1983 in Gateway Design Automation to model hardware at various levels, developed with a simulator
- Verilog synthesis tool from Synopsys, 1987
- Gateway Design Automation → Cadence, 1989
- Verilog made public domain to compete with VHDL; standards in 1995, 2001, 2005


# Digital Design Using An HDL

- **Circuit Under Design (CUD)**  
(modeled using an HDL)
- **Test Bench**
  - Inputs (**stimulus**) to CUD
  - Simulation of the CUD
  - Method for checking outputs
- **Coverage**  
(how much is really tested?)
- Generally, an iterative process...

# Typical Digital Design Flow

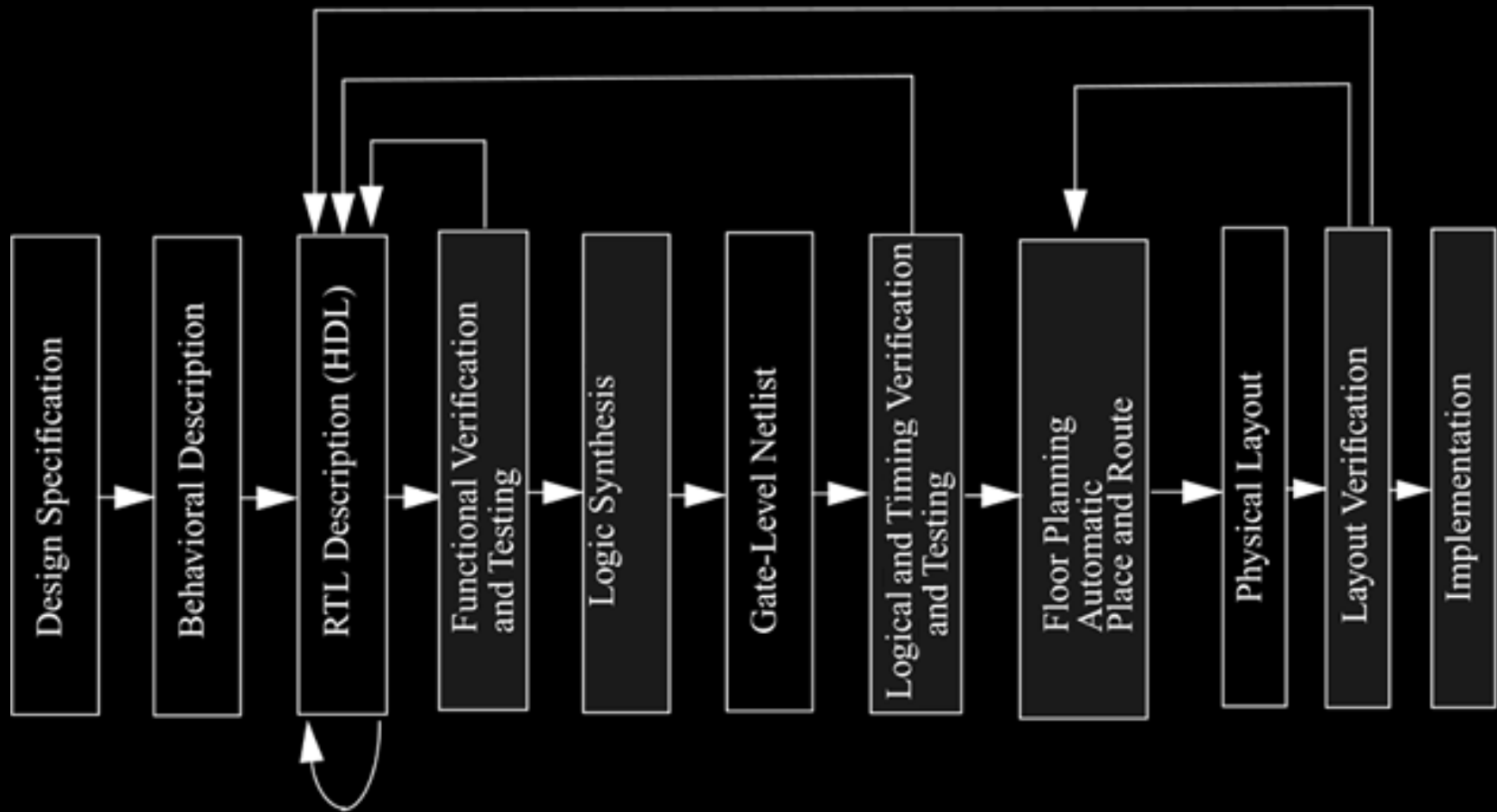

# Digital Design Methodology

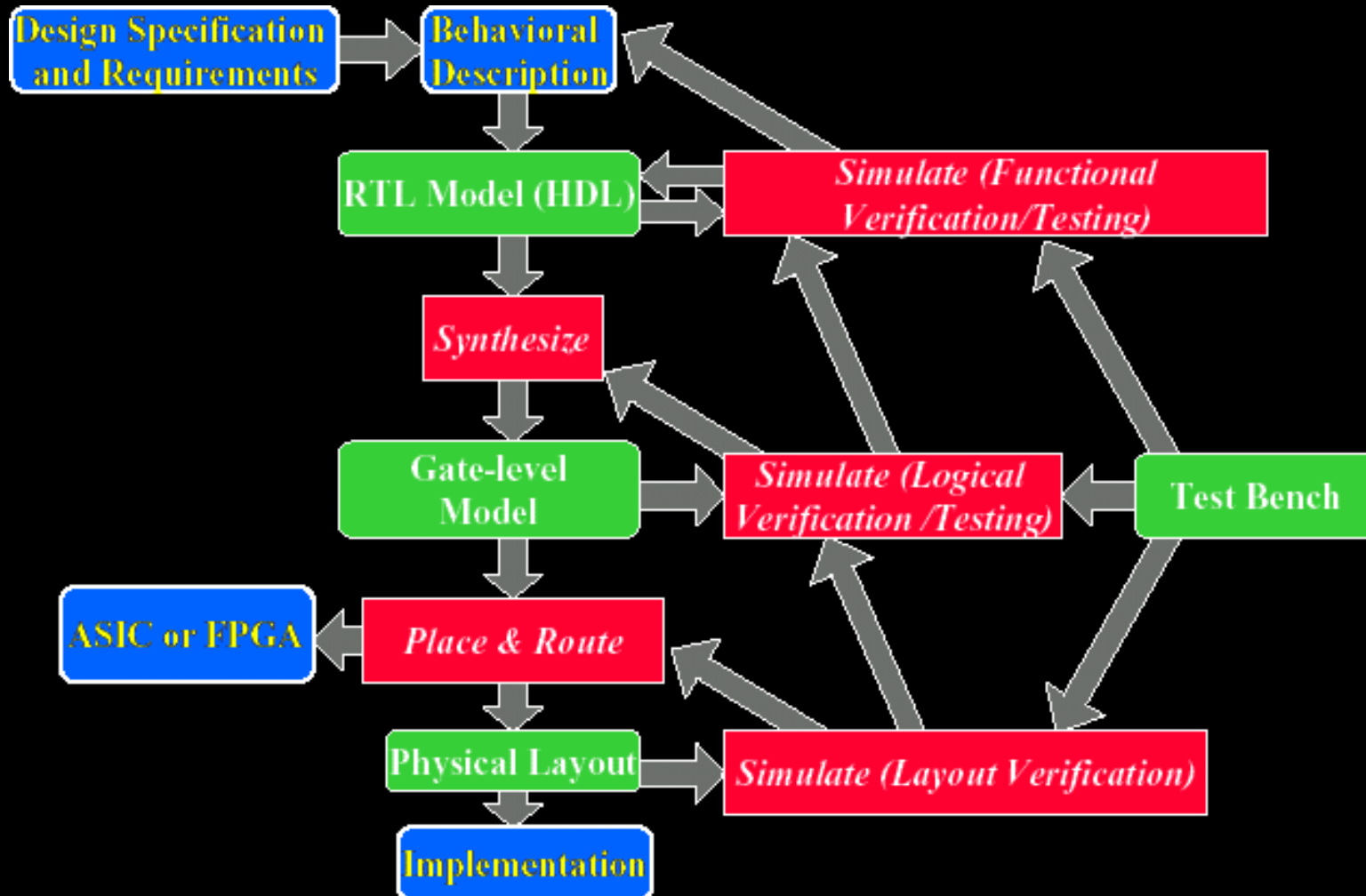

# Verilog Hello, World!

- You can do things at a high enough level so that Verilog is just a programming language:

```
module helloworld;  
  initial  
    $display("Hello, World!");  
endmodule
```

- That will not get hardware built!

# Synthesizable Verilog

- Defines and instantiates hardware modules:

```
module not_gate(in, out);  
    input in;  
    output out;  
    // ain't Verilog neat!  
    assign out = ~in;  
endmodule
```





# Module Nesting

- Can instantiate a module inside a module
- Cannot define a module inside a module

i.e., it works just like C...

# Parametric Module Content

- A module specifies a chunk of hardware, but it **can be parameterized in various ways**
- Constant values can be **parameters**
- Can **generate** structures at compile time using **genvar** variables

# Parameter Example

```
module lsbof(dout, din);  
parameter BITS=4;  
output dout; input [BITS-1:0] din;  
assign dout = din[0];  
endmodule
```

```
module tryit;  
reg [7:0] b = 42; wire a;  
lsbof #(8) mylsb(a, b);  
initial #1 $display(a);  
endmodule
```

```
// instead of #(8), could have said  
lsbof #(.BITS(8)) mylsb(a, b); // or elsewhere said  
defparam tryit.mylsb.BITS = 8;
```

# Parameter Example

- `tryit` only tries one input value
- Can run it here:  
<http://aggregate.org/EE480/parameter.html>

# A 4-bit Odd Parity Module

```
module parity4(dout, din); // compute odd parity
output dout; input [3:0] din;
wire [3:0] tmp; assign tmp[0] = din[0];
xor mygate1(tmp[1], tmp[0], din[1]);
xor mygate2(tmp[2], tmp[1], din[2]);
xor mygate3(tmp[3], tmp[2], din[3]);
assign dout = tmp[3];
endmodule
```

```
module tryit;
reg [3:0] b = 7; wire a;
parity4 myparity(a, b);
initial #1 $display(a);
endmodule
```

# 4-bit Odd Parity Example

- `tryit` only tries one input value
- Can run it here:  
<http://aggregate.org/EE480/oddparity4.html>

# Generate BITS-bit Odd Parity

```
module parity(dout, din); // compute odd parity
parameter BITS=4;
output dout; input [BITS-1:0] din;
wire [BITS-1:0] tmp; assign tmp[0] = din[0];
genvar i;
generate for (i=1; i<BITS; i=i+1) begin:xors
    // xor gates named xors[i].mygate
    xor mygate(tmp[i], tmp[i-1], din[i]); end endgenerate
assign dout = tmp[BITS-1];
endmodule
```

```
module tryit;
reg [7:0] b = 42; wire a;
parity #(8) myparity(a, b);
initial #1 $display(a);
endmodule
```



# BITS-bit Odd Parity Example


- `tryit` only tries one input value
- Can run it here:  
<http://aggregate.org/EE480/oddparity.html>

# Verilog Abstraction Levels


- **Behavioral** (algorithmic) level
  - programming, sort of
- **Dataflow** level
  - data flow between registers and processing
- **Gate** level
  - connecting logic gates
- **Switch** level
  - interconnecting (MOS) transistors
- **Register-Transfer Level (RTL)**
  - Behavioral + dataflow that is **synthesizable**

# Hierarchical Modeling


- Top down

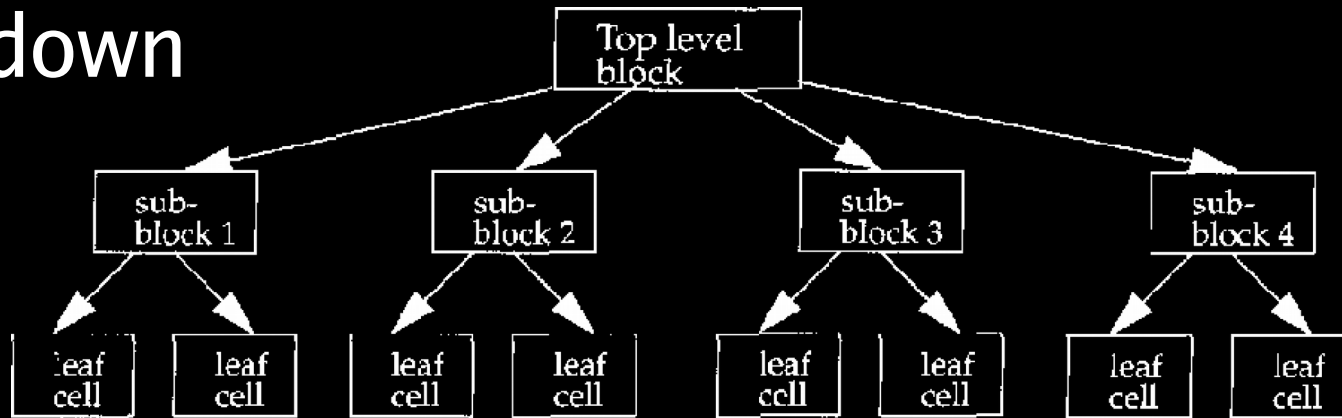


- Bottom up

 

# 4-bit Ripple Carry Counter

 


# Ripple Counter Hierarchy

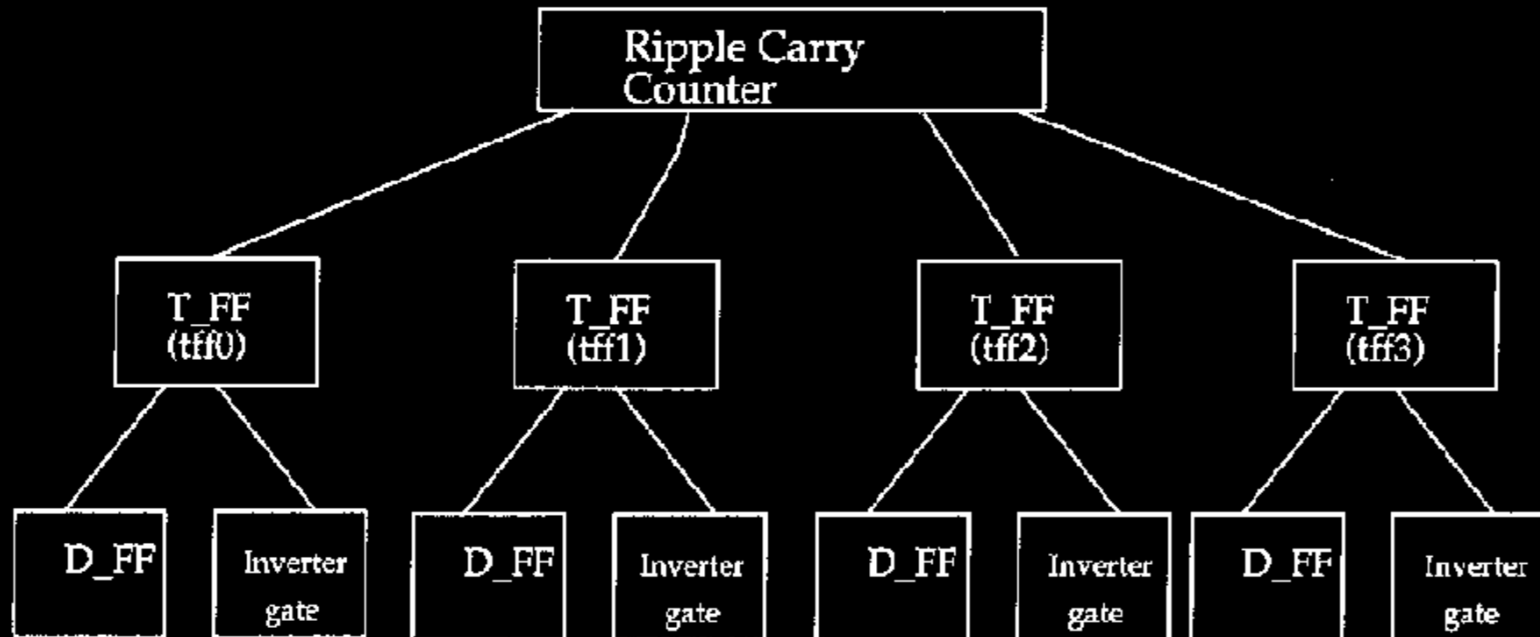

# T-Filp-Flop

reset	$q_n$	$q_{n+1}$
1	1	0
1	0	0
0	0	1
0	1	0

 

# D-Flip-Flop Module


- Make a T from a D...

```
module DFF(q, d, clk, reset);  
  input d, clk, reset;  
  output q;  
  reg q; // q is a register  
  always @(posedge reset or  
          negedge clk)  
    if (reset) q = 1'b0; else q = d;  
endmodule
```
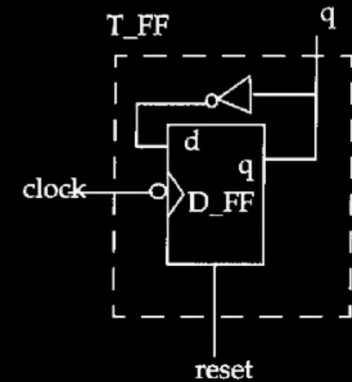
# T-Flip-Flop Module


- Make a T from a **DFF** instance

```
module TFF(q, clk, reset);  
  input clk, reset;  
  output q;  
  wire d; // d is an internal wire  
  DFF dff0(q, d, clk, reset);  
  not n1(d, q); // use built-in not  
endmodule
```






# Ripple Counter From 4 TFFs

 


```
module ripcount(q, clk, reset);  
    input clk, reset;  
    output [3:0] q; // 4-bit output  
    TFF tff0(q[0], clk, reset);  
    TFF tff1(q[1], q[0], reset);  
    TFF tff1(q[2], q[1], reset);  
    TFF tff1(q[3], q[2], reset);  
endmodule
```

# Test Bench Styles

- Stimulus instantiates design

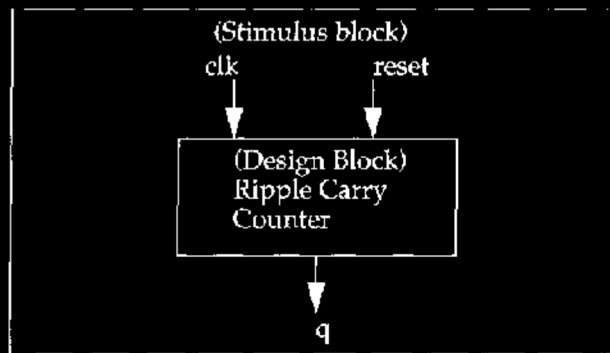


- Dummy module instantiates both

 


# Example Design & Stimulus

- Stimulus and output waveforms

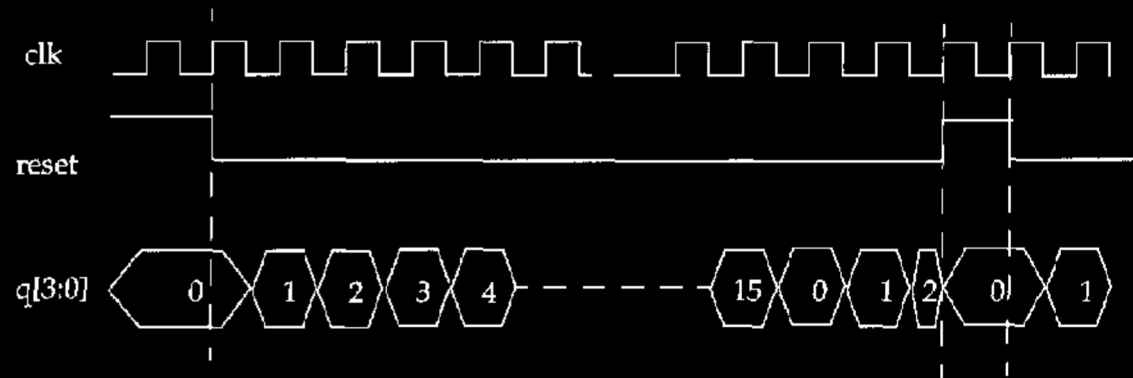

- Design block

 

# Ripple Counter Stimulus

```
module stimulus;
  reg clk; reg reset; wire[3:0] q;
  ripcount r1(q, clk, reset);
  initial clk = 1'b0;
  always #5 clk = ~clk; // flip clk every 5 ticks
  initial // drive the reset signal sequence
  begin
    reset = 1'b1;
    #15 reset = 1'b0;
    #180 reset = 1'b1;
    #10 reset = 1'b0;
    #20 $stop; // end simulation
  end
  initial // output a trace
    $monitor($time, " Output q = %d", q);
endmodule
```

# Ripple Counter

- Need a test framework to try it out...
  - `stimulus` module instantiates `ripcount`
  - Stimulus initializes values, generates clock, and prints results each time they change
- Can run it here:

<http://aggregate.org/EE480/ripplecount.html>

# Verilog

## As A Programming Language

(maybe your first **parallel** programming language)

# Verilog Comments

- Both C comment styles are supported:

// to end of this line is ignored

/\* to matching close  
is ignored \*/

# Verilog Names

- Similar to C in many ways:
  - All keywords are lowercase
  - Names can use `a-z`, `A-Z`, `0-9`, `_`
  - Names don't start with `0-9`
  - Only system task names can start with `$`
  - Whitespace generally treated as a separator
- Escaped identifiers start with `\` and end with whitespace... e.g.:

`\*@#$$%&! //` is the name `*@#$$%&!`



# Verilog Numbers

- Precision (in bits) can be explicit:
  - Prefix *size*' specifies *size* bits precision
  - Unsized is at least 32 bits (' optional)
- Base defaults to 10, but can be specified:
  - Hexadecimal (base 16): **h** or **H**
  - Decimal (base 10): **d** or **D**
  - Octal (base 8): **o** or **O**
  - Binary (base 2): **b** or **B**
- E.g.: 255 'Hff 8'o377 8'b11111111

# Verilog X And Z Values

- Used with base 2, 8, or 16 constants
- An unknown value is (lowercase): `x`
  - Number of bits in `x` determined by base
  - E.g.: `8'b1010xxxx` `8'hax`
- A high-impedance value is (lowercase): `z`
  - Number of bits in `z` determined by base
  - E.g.: `8'bz z z z xxxxx` `8'hzx`
- Extending precision pads with: `x z 0`  
e.g.: `4'bxx` `4'hx` ; `4'b1x` `4'b001x`

# Other Value Oddities

- In numbers:
  - `?` can be used in place of `z`
  - `_` is ignored (but can't start a number)
  - E.g.: `8'h2_?` `8'b0010zzzz`
- Negative numbers:
  - Always treated as 2's complement
  - Sign before precision: `-8'1` *not* `8'-1`

# Strength Levels

Strength level	Type	Degree
supply	Driving	 strongest
strong	Driving	
pull	Driving	
large	Storage	
weak	Driving	
medium	Storage	
small	Storage	
highz	High Impedance	

# Verilog Wires (Nets)

- Wires represent *potential* connections between hardware elements; signals that are continuously driven
- Keyword: `wire tri wand tri0 tri1`
- Default value: `z` (or given default `0` or `1`)
- Can specify width

```
wire myoutput; // a wire
tri [31:0] mybus; // tri-state bus
wand myand; // a wired-AND
```

# Verilog Registers

- Registers represent data storage elements... like variables (not edge-triggered, clocked)
- Retain (*unsigned*) value until next assignment
- Keyword: `reg trireg`
- Default value: `x`
- Can specify width (default at least 32):

```
reg [15:0] r; // r is a 16-bit reg
```

# Verilog Integers

- Integers are basically *signed* registers
- Keyword: `integer`
- Can specify width (default at least 32)
- Two equivalent declarations:

```
integer [15:0] r;
```

```
reg signed [15:0] r;
```

# Verilog Reals

- Reals are floating-point values
  - Can use decimal: 3.14
  - Can use scientific notation: 314e-2
- Keyword: `real`
- Default value: 0
- Value is rounded when you need an integer

```
real r;
```



# Verilog Times

- Times hold values of (simulated) time
- Keyword: `time`
- Precision is at least 64 bits
- `$time` system variable gives the current time

```
time when_started;  
initial  
    when_started = $time;
```

# Verilog Vectors

- A vector specifies multiple-bit width
- Applies to `reg integer wire`
- Specifies range and order:  
`[msb_index : lsb_index]`
- Can select a bit or a subset of bits

```
wire [31:0] mybus;  
reg [0:31] reversed;  
mybus[15:0] // not mybus[0:15]  
reversed[16] // just bit 16
```

# Verilog Variable Vector Select

```
reg [255:0] data1; // little endian
reg [0:255] data2; // big endian
reg [7:0] byte;

// variable part select, fixed 8-bit width
byte = data1[31 -: 8]; // data1[31:24]
byte = data1[24 +: 8]; // data1[24:31]
byte = data2[31 -: 8]; // data2[31:24]
byte = data2[24 +: 8]; // data2[24:31]

// start bit pos can be a variable (but not width)
for (j=0; j<=31; j=j+1)
    byte = data1[(j*8) +: 8]; // [7:0], [15:8], ...

// initialize only part of a vector
data1[(bytenum*8) +: 8] = 8'b0;
```

# Verilog Arrays

- An array specifies *multi-dimensional* collections
- Applies to all data types
- Specifies range and order:  
[ *start\_index* : *end\_index* ]
- **Cannot slice, can only select an element**
- Syntactically declared after identifier,  
but any vector subscripting comes last in use

```
wire [31:0] mybusses [0:4];  
mybusses[2][15:0] // bus 2, 16 lsbs
```

# Verilog Array Examples

```
integer count[0:7];  
reg bool[31:0];  
time chk_point[1:100];  
reg [4:0] port_id[0:7];  
integer matrix[4:0][0:16];  
wire [7:0] w_array[5:0];  
count[5] = 0;  
port_id[3] = 0;  
matrix[1][0] = 601;  
port_id = 0; // illegal!  
matrix[1] = 0; // illegal!
```

# Verilog Memories

- RAM, ROM, and register files are all basically modeled as arrays of `reg`  
(synthesis is complicated using RAM blocks...)
- Word size for a memory is vector size, number of elements is array size
- Selecting an array element is basically a decoder/mux structure...

```
// memory holding 65536 bytes  
reg [7:0] myram[0:'hffff];
```

# Verilog Strings

- Strings look like they do in C:
  - Surrounded by double-quotes
  - Escapes: `\t \n \" \\ \oct %%`
  - E.g.: `"Hello, World!\012"`
- Mostly used for arguments to system tasks
- Also can be `reg` vector initializers filling 8 bits/char from least to most significant

```
Reg [32*8:1] mystring;  
mystring = "Hello, World!\n"
```

# Verilog Operators

- Arithmetic: + - \* / %
- Relational: < <= > >=
- Logical equality: == !=
- Case equality: === !==

```
assign a = (1 == 1); // a = 1
```

```
assign b = (1 == 1'bx); // b = x
```

```
assign c = (1'bx === 1'bx); // c = 1
```



# Verilog Operators

- Logical: `! && ||`
- Bitwise: `~ & | ^ ~^` (xnor)
- Unary reduction: `& ~& | ~| ^ ~^`
- Shift: `>> <<` (always 0 filled)

```
assign a = (& 3'b010); // a = 0
assign b = (& 3'bz11); // b = x
assign c = (3'b110 >> 1); // c = 3
```

# Verilog Operators

- Trinary conditional: `? :`
- Concatenation: `{ }`
- Replication: `{ { } }`

```
assign a = (1 ? 1'bx : 0); // a = x
assign b = {1'1 , 1'0}; // b = 'b10
assign c = {2{a,b}}; // c = {a,b,a,b}
```

# Verilog Gate Level


- Built-in: `and nand nor or xor xnor`
  - 1<sup>st</sup> argument is output, then inputs
- Built-in: `buf not` (drivers)
  - Any number of output arguments, then last is the only input
  - Any `z` input becomes an `x` output

```
and a(out1, in1, in2);
```

```
buf b(out2, out3, out4, in3);
```
 
# Gate Level 1-of-4 Mux

```
module mux1of4 (Z, D0, D1, D2, D3, S0, S1);  
output Z;  
input D0, D1, D2, D3, S0, S1;  
not (S0bar, S0), (S1bar, S1);  
and (T0, D0, S0bar, S1bar),  
    (T1, D1, S0bar, S1),  
    (T2, D2, S0, S1bar),  
    (T3, D3, S0, S1);  
// should be or, not nor  
or (Z, T0, T1, T2, T3);  
endmodule
```



# Gate-Level 1-of-4 Mux Example

- `tryit` only tries one input value

- Can run it here:

<http://aggregate.org/EE480/mux1of4.html>

# Verilog Data Flow Modeling

- Uses **continuous assignment**: `assign`
  - Lval: a net, part of a net, or concatenation
  - Rval is re-evaluated when anything changes

```
wire[7:0] a, b, c;  
wire[15:0] big;  
assign {b, c} = big;  
assign a=b&c;
```

# Verilog Delay Modeling

- Delay between rval change and lval update
- Specified in units of `time`
  - Delay in individual `assign #delay`
  - Property of a `wire #delay`
- Changes faster than `delay` are skipped

```
wire #5 [7:0] a;  
wire [7:0] b, c;  
assign #2 b=c; // delayed 2  
assign a=c; // delayed 5
```

# Verilog Behavioral Modeling

- Procedural blocks:
  - All activate at time 0
  - All execute concurrently
  - `initial` blocks execute only at time 0
  - `always` blocks execute repetitively, as specified, e.g.: `always@(posedge clk)`
- Mostly about changing `reg` values
- `begin` and `end` can group statements



# Always Procedural Timing

- `always ( timing_control )`
  - An `or` of identifiers
  - `posedge` of an identifier (`0→1`)
  - `negedge` of an identifier (`1→0`)
  - `#` time delay expression (make a waveform)

```
reg clk;  
always @(posedge clk) begin ... end  
always #5 clk = ~clk;
```

# Procedural Assignments

- Usable in `initial` or `always` blocks
- Lval must be a `reg integer` ...
- Two different assignment operators:
  - For a wire: `=`
  - For a flip-flop: `<=`
- Wire assignments can be instantaneous, but flip-flops distinguish before and after state

# Procedural Assignments

```
always @(A or B) // infer wire
begin
    B=A; C=B;
end
```

```
Always @(posedge CLK) // flip-flop
begin
    B<=A; C<=B; D<=C;
end // clock skew! (may be ok?)
```

# Conditional Statements

- `if (expr) stat`  
`if (expr) stat else stat`
- `case (expr) cases endcase`  
A case is: `values : stats`  
Can have a: `default: stats`
- For grouping: `begin ... end`

# Looping Statements

- `while (expr) stat`

Just like C

- `for (expr ; expr ; expr) stat`


Note: no `++` operator, so `++i` is `i=i+1`

- `repeat (expr) stat`


Not like C – repeat `stat` `expr` times

- `forever stat`

# A Big Example: A Multiplier

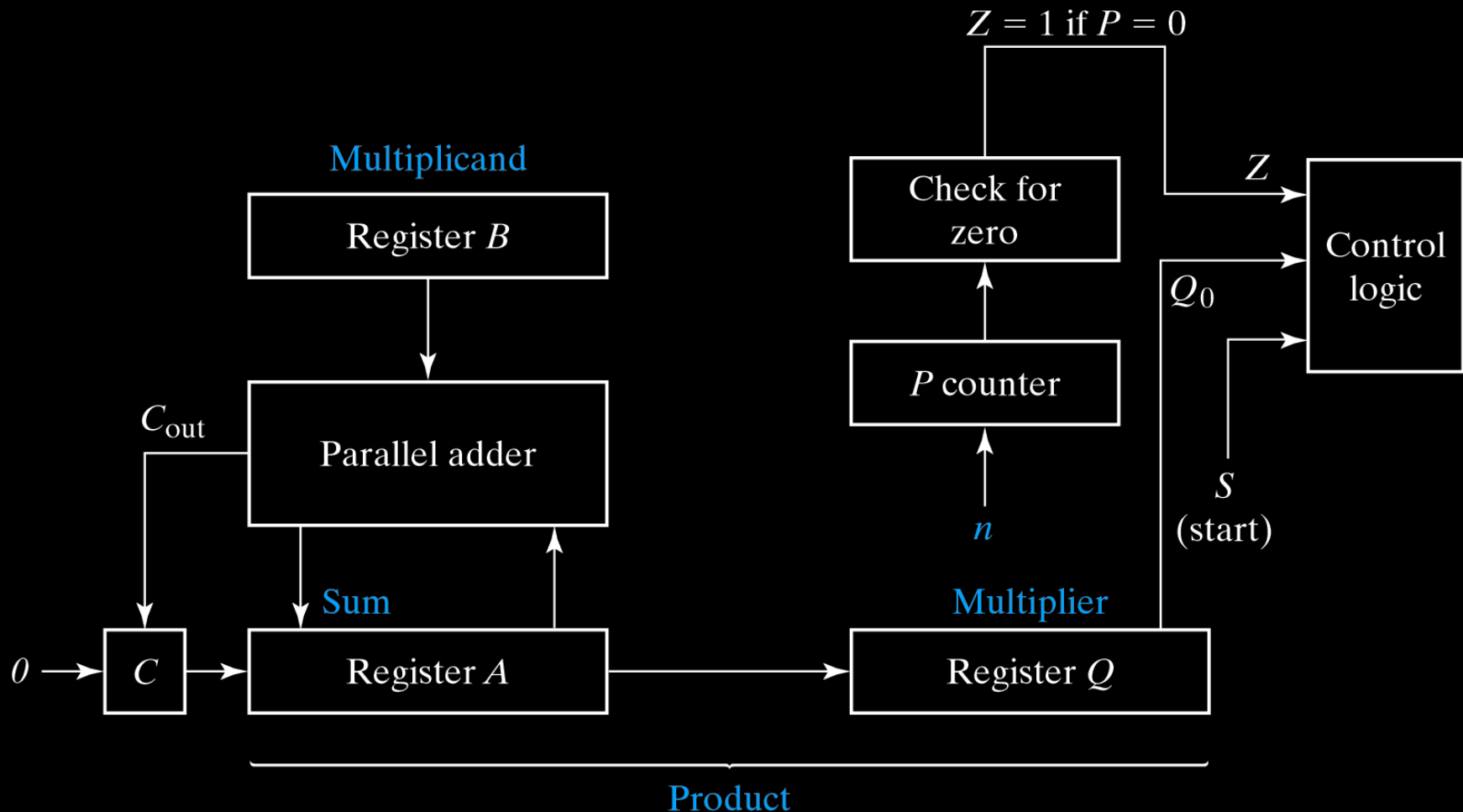

# Multiplier State Machine Flowchart

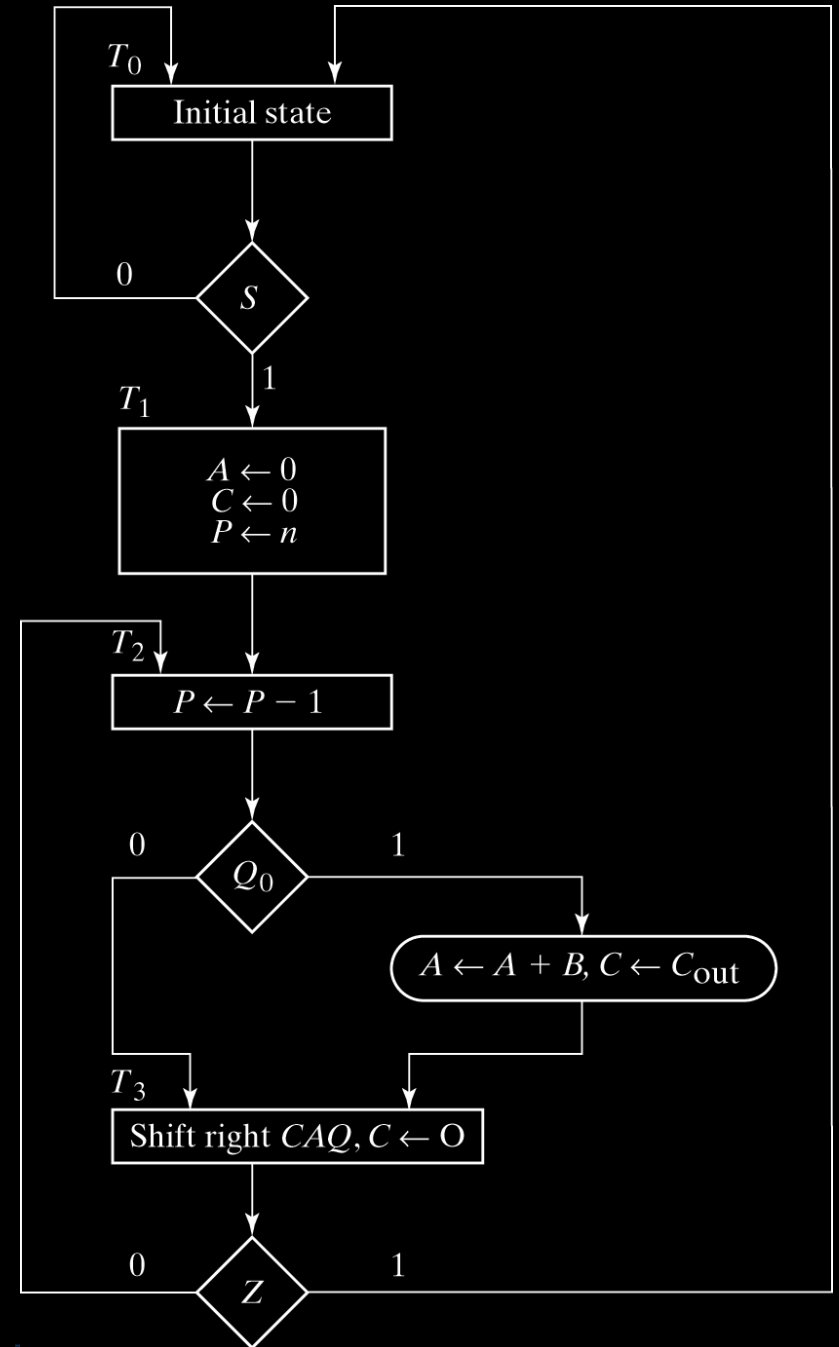


# Example Trace Of Multiply

Multiplicand B = 1011				
	C	A	Q	P
Multiplier Q	0	00000	10011	101
$Q_0 = 1$ ; 加 B		10111		
<b>First partial product</b>	0	10111		100
Shift right CAQ	0	01011	11001	
$Q_0 = 1$ ; add B		10111		
<b>Second partial product</b>	1	00010		011
Shift right CAQ	0	10001	01100	
$Q_0 = 0$ ; shift right CAQ	0	01000	10110	010
$Q_0 = 0$ ; shift right CAQ	0	00100	01011	001
$Q_0 = 1$ ; add B		10111		
<b>Fifth partial product</b>	0	11011		
Shift right CAQ	0	01101	10101	000
Final product in AQ = 0110110101				



# Multiplier Control Logic

 


$T_0$ : Initial state

$T_1$ :  $A=0$ ,  $C=0$ ,  $P=n$

$T_2$ :  $P=P-1$

$T_3$ : Shift CAQ right,  $C=0$

# Multiplier Control Block

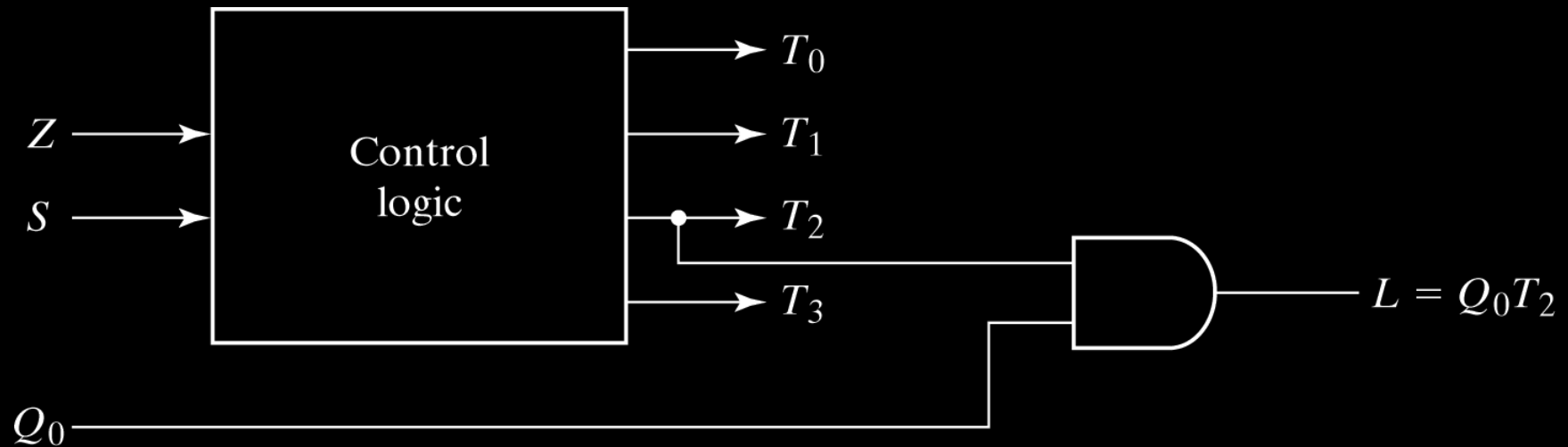


$L$  is the signal that latches the add result in state  $T_2$  when  $Q_0$  is a 1.

# Assign State Numbers


State assignment for control			
State	Binary	Gray code	One-hot
$T_0$	00	00	0001
$T_1$	01	01	0010
$T_2$	10	11	0100
$T_3$	11	10	1000

Present state		Input		Next state		Output			
$G_1$	$G_0$	S	Z	$G_1$	$G_0$	$T_0$	$T_1$	$T_2$	$T_3$
0	0	0	X	0	0	1	0	0	0
0	0	1	X	0	1	0	1	0	0
0	1	X	X	1	0	0	0	1	0
1	0	X	X	1	1	0	0	0	1
1	1	X	0	1	0	0	0	1	0
1	1	X	1	0	0	1	0	0	0

# Control Logic Diagram

 

# Control Logic Diagram

 

# Verilog Multiplier

```
module mulBiQi(S,Clk,Clr,Bi,Qi,C,A,Q,P);
input S,Clk,Clr; input[4:0]Bi,Qi;
output C; output[4:0]A,Q; output[2:0]P;
reg C; reg[4:0]A,Q,B; reg[2:0]P; reg[1:0]ps,ns;
parameter T0=2'b00,T1=2'b01,T2=2'b10,T3=2'b11;
wire Z;
assign Z= ~|P; // nor reduction of P
always @(negedge Clk or negedge Clr)
    if (~Clr) ps=T0; else ps<=ns;
always @(S or Z or ps)
    case (ps) // next state logic
        T0: if (S) ns=T1; else ns=T0;
        T1: ns=T2;
        T2: ns=T3;
        T3: if (Z) ns=T0; else ns=T2;
    endcase
```

# Verilog Multiplier (continued)

```
always @(negedge Clk)
  case (ps) // next state logic
    T0: B<=Bi; // get multiplicand
    T1: begin // get multiplier, counter to 5 (bits)
      A <= 5'b00000; C <= 1'b0; P<=3'd5; Q<=Qi; end
    T2: begin // do add (verilog builds the adder!)
      P<=P-3'b001; if (Q[0]) {C,A}<=A+B; end
    T3: begin // shifts
      C<=1'b0; A<={C,A[4:1]}; A<={A[0],Q[4:1]}; end
  endcase
endmodule
```



# Verilog Multiplier Test Bench

```
module test_mulBiQi;
reg S,Clk,Clr; reg[4:0]Bi,Qi;
wire C; wire[4:0]A,Q; wire[2:0]P;
mulBiQi mp(S,Clk,Clr,Bi,Qi,C,A,Q,P);
initial begin
    S=0; Clk=0; Clr=0;
    #5 S=1; Clr=1; Bi=5'b10111; Qi=5'b10011;
    #15 S=0; end
initial begin
    repeat (26) #5 Clk = ~Clk;
end
always @(negedge Clk)
    $strobe("C=%b A=%b Q=%b P=%b time=%0d",C,A,Q,P,$time);
endmodule
```


# Multiplier Example

- Can run it here:  
<http://aggregate.org/EE480/multiplier.html>
- But that's rather convoluted...  
So how about the multiplier from EE380?
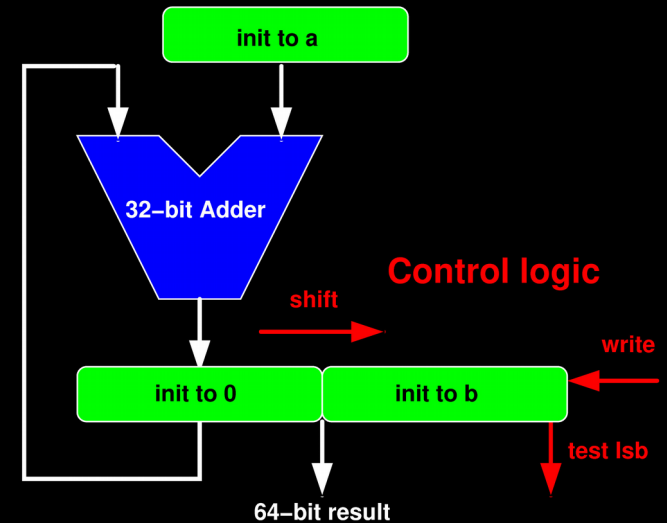
# EE380 Multiplier Example


```
module mul(ready, c, a, b, reset, clk);
```

```
parameter BITS = 32;  
input [BITS-1:0] a, b;  
input reset, clk;  
output reg [BITS*2-1:0] c;  
output reg ready;  
reg [BITS-1:0] d;  
reg [BITS-1:0] state;  
reg [BITS:0] sum;
```


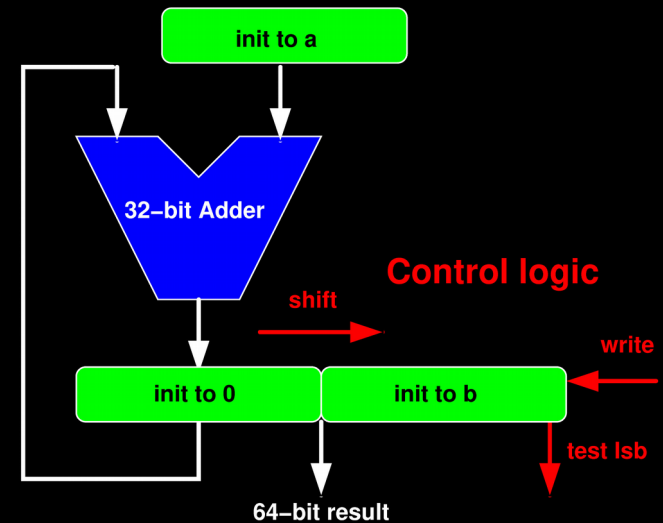
# EE380 Multiplier Example


```
always @(posedge clk or posedge reset) begin
  if (reset) begin
    ready <= 0;
    state <= 1;
    d <= a;
    c <= {{BITS{1'b0}}, b};
  end else begin
    if (state) begin
      sum = c[BITS*2-1:BITS] + d;
      c <= (c[0] ? {sum, c[BITS-1:1]} :
            (c >> 1));
      state <= {state[BITS-2:0], 1'b0};
    end else begin
      ready <= 1;
    end
  end
end
endmodule
```


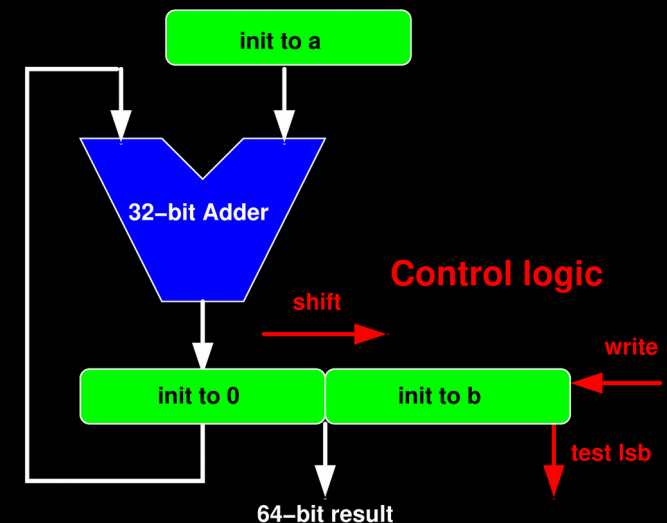
# EE380 Multiplier Example

```
module tryit;
reg [7:0] a, b;
wire [15:0] c;
wire rdy;
reg reset, clk;

mul #(8) mymul(rdy, c, a, b, reset, clk);
initial begin
    A = 6; b = 7;
    Clk = 0; reset = 0;
    #1 reset = 1;
    #1 reset = 0;
    repeat (20) begin
        #1 clk = ~clk;
        #1 $display(a, " * ", b, " = ", c, " done=", rdy);
    end
end
endmodule
```



# EE380 Multiplier Example

- Can run it here:  
<http://aggregate.org/EE480/mul380.html>
- Notice that we only bother with 8 bits...  
using the parameter to restrict the 32-bit design